

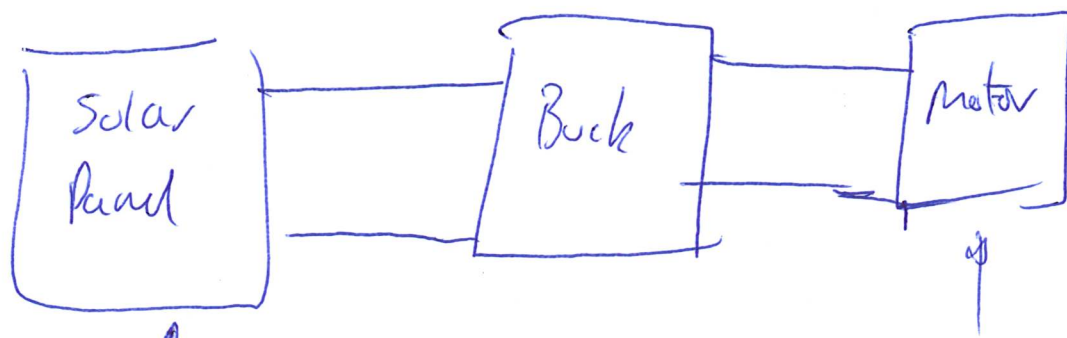
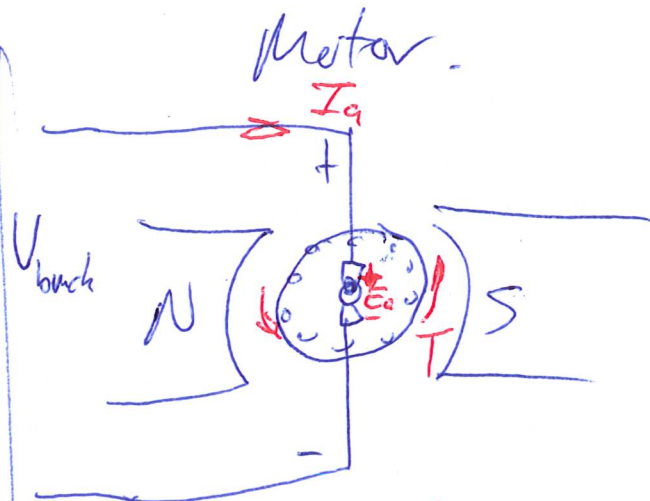


# Solar Car Project.

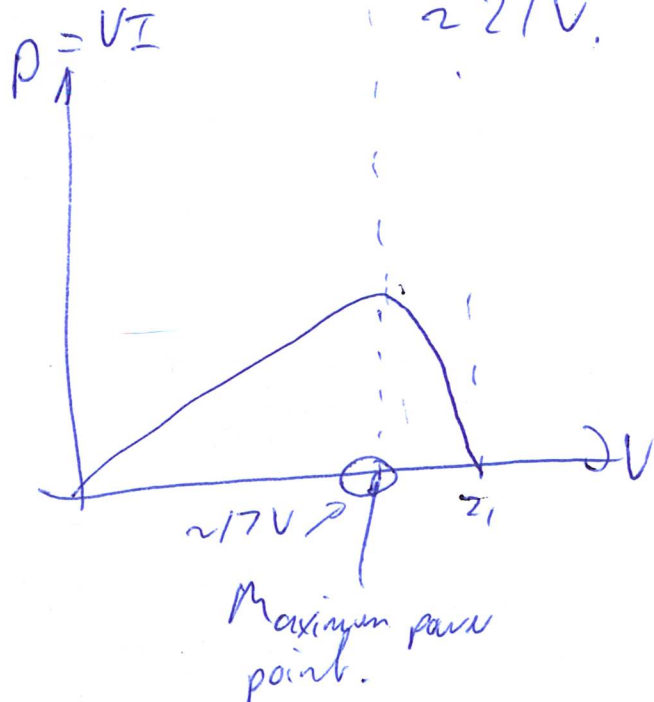

Maximum power  
at all times  
→ Maximum power-point

Characteristics

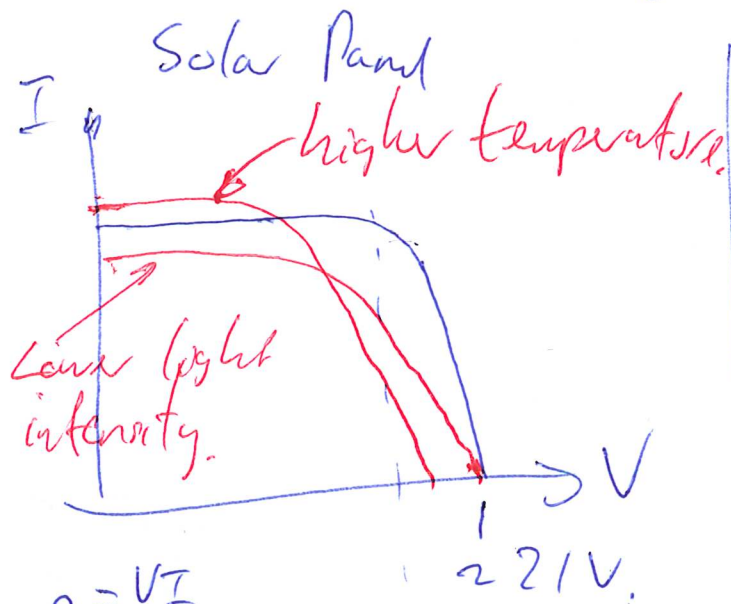


$$E_a = k\omega$$

$$T = kI_a$$

From standstill need 1.5-2A  
to start turning.  
 $V_{buck} \sim 2V$ .

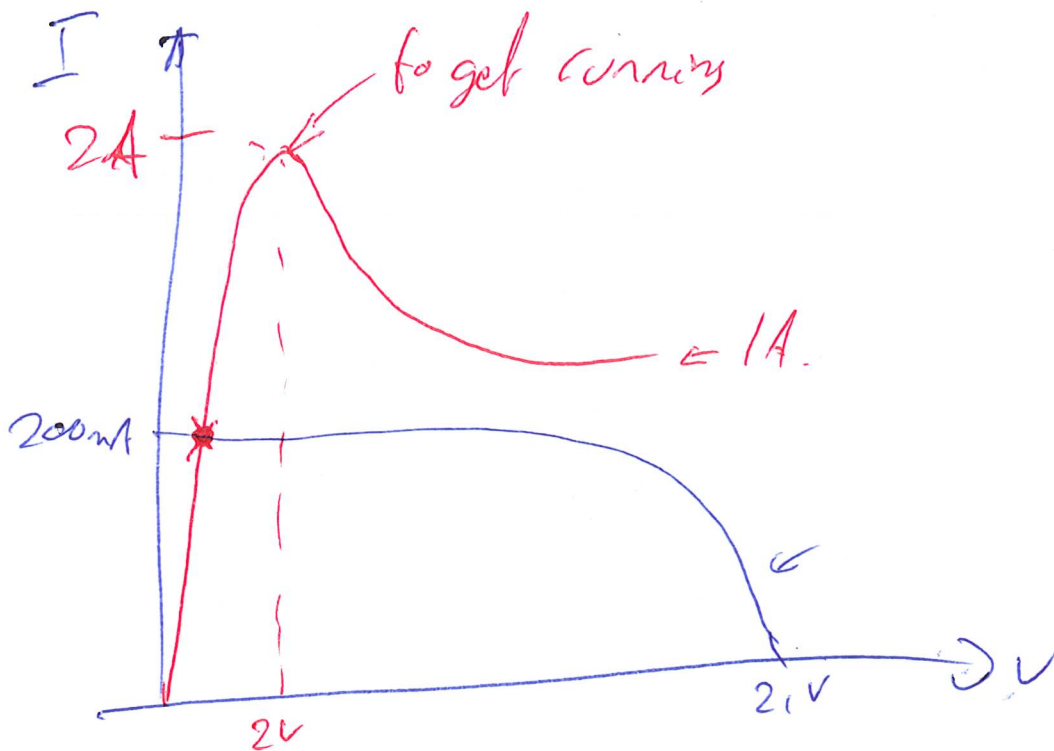For running  
need  $\sim 1A$  at  $V_{buck} \sim 6$  or  $7V$



A buck converter acts in concept as a dc transformer.

High  $V_{in}$   
Low  $I_{in}$



Low  $V_{out}$   
high  $I_{out}$

$$P_{in} = P_{out}$$

